



**Course:** Digital Logic Design  
**Program:** BS (Computer Science)  
**Duration:** 15 Minutes  
**Paper Date:** 09/04/2022  
**Section:** 2N  
**Exam:** Quiz 3


**Course Code:** EE-227  
**Semester:** Spring-2022  
**Total Marks:** 10  
**Weight**  
**Page(s):** 3  
**Roll No.**

**Instruction/Notes:** Calculators are strictly not allowed in all exams  
 Plagiarism will be dealt seriously causing an F in
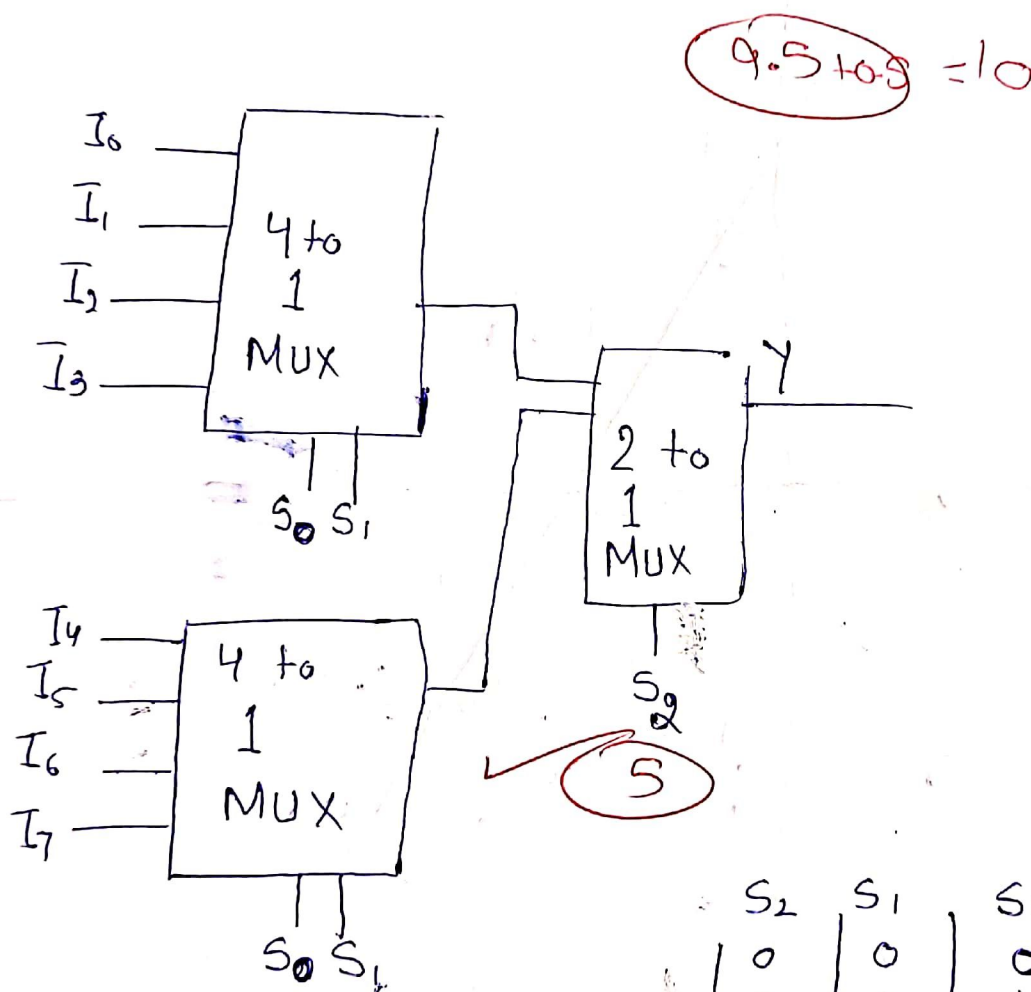
## Question 01:

[5 M]

Design an 8-to-1-line multiplexer using two 4-to-1-line multiplexers and one 2-to-1-line multiplexer.



S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

**Question 02:**

Implement the Boolean function  $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$  with a 4-to-1-line multiplexer and external gates. Connect inputs A and B to the selection lines. The input requirements for the four data lines will be a function of the variables C and D. The values of these variables are obtained by expressing F as a function of C and D for each of the four cases when AB = 00, 01, 10 and 11. These functions must be implemented with external gates.

Selection lines.

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
<hr/>				
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
<hr/>				
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
<hr/>				
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1



$$F = D$$

$$F = (C+D)'$$

$$F = CD$$

$$4.5 + 0.5$$

$$F = 1$$

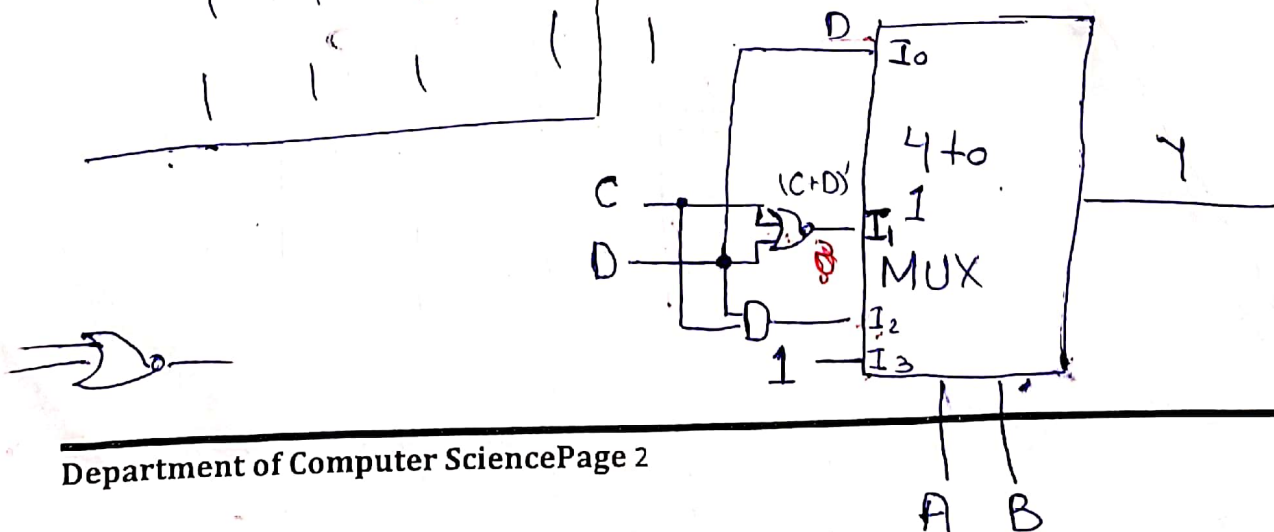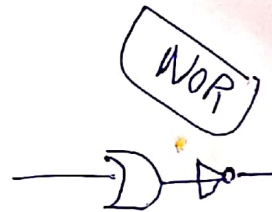

# National University of Computer and Emerging Sciences, Lahore Campus



Course:

Digital Logic Design

Course

Code: EE227

Program:

BS(Computer Science, Data Science)

Semester:

Spring 2022

Duration:

60 Minutes

Total Marks:

50

Paper Date:

09 - May - 2020

Weight

15%

Section:

ALL

Page(s):

5

Exam:

Midterm-II

Section:


Name:

Roll No.

- Instruction/Notes:
- Attempt all the questions on this answer booklet. You can use extra sheets for your scratch work but **these will not be collected and marked.**
  - Make sure you write your roll # on EVERY sheet of the booklet.

Question Number:	Q. 1	Q. 2	Q. 3	Total
Marks:	10	20	20	50
Marks Obtained:	09	20	20	49

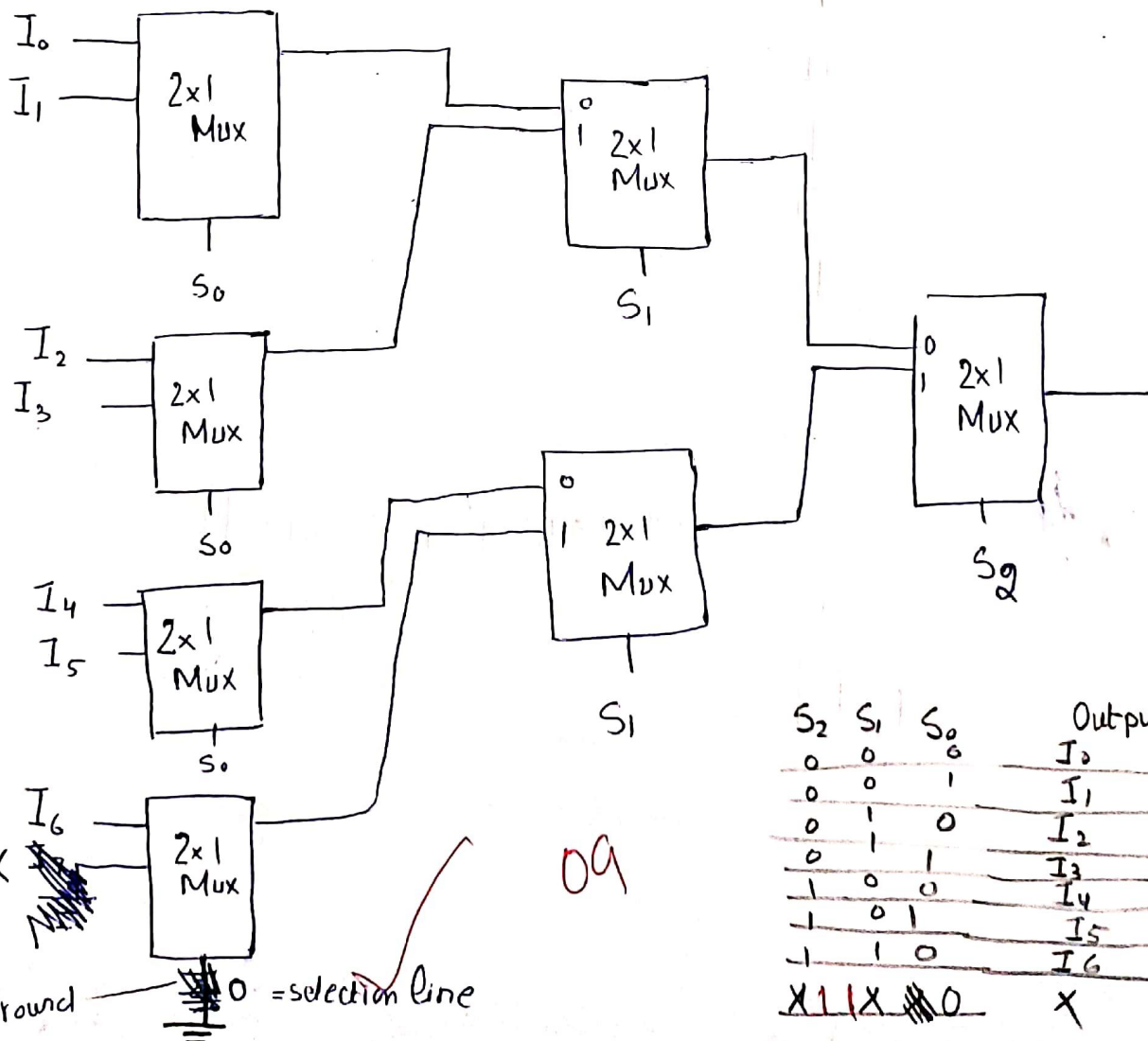**Question 1:** Construct a 7-to-1-line multiplexer with as many 2-to-1-line multiplexers as are needed. [10]



## Question 2:

A new type of flip-flop, **GH flip-flop** (GH F/F) has been introduced that has four operations as shown in Table 1.

Use the given space to

(a) Tabulate the characteristic table. [5]

(b) Derive the characteristic equation [5]

(c) Tabulate the excitation table. [10]

G	H	Function
0	0	Clear to 0
0	1	No change
1	0	Complement
1	1	Set to 1

Clear = 0  
Q = 0

**Table 1:** Function table of GH F/F

Q(t)	G	H	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Q(t)	Q(t+1)	G	H
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

**Table 3:** Excitation table of GH F/F

**Table 2:** Characteristic table of GH F/F

### Derivation of Characteristic Equation:

Q(t) \ GH	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Q(t+1) = Q(t)'G + Q(t)H$$



**Question 3:** Two Boolean functions **F** and **G** are described as

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 8, 10, 11, 13, 14, 15)$$

$$G(A, B, C, D) = \prod M(1, 2, 3, 7, 8, 12, 13, 15)$$

[4]

(a) Fill-in the entries in the table below for **F** and **G**.

Inputs					Outputs	
	A	B	C	D	F	G
0	0	0	0	0	1	1
1	0	0	0	1	1	0
2	0	0	1	0	1	0
3	0	0	1	1	0	0
4	0	1	0	0	1	1
5	0	1	0	1	1	1
6	0	1	1	0	0	1
7	0	1	1	1	1	0
8	1	0	0	0	1	0
9	1	0	0	1	0	1
10	1	0	1	0	1	1
11	1	0	1	1	1	1
12	1	1	0	0	0	0
13	1	1	0	1	1	0
14	1	1	1	0	1	1
15	1	1	1	1	1	0

$$F = \overline{C}D$$

$$F = \overline{C}D$$

$$F = C' + D$$

$$F = C' + D$$

$$F = C + D'$$

$$F = C + D'$$

$$F = C + D$$

$$F = C + D$$

$$2^2$$

C	D	0	1
0		1	1
1		1	

$$\overline{C} + \overline{D}$$

C	D	0	1
0		1	1
1			1

$$C' + D$$


C	D	0	1
0		1	
1			1

$$D' + C$$

C	D	0	1
0			1
1		1	1


$$C + D$$

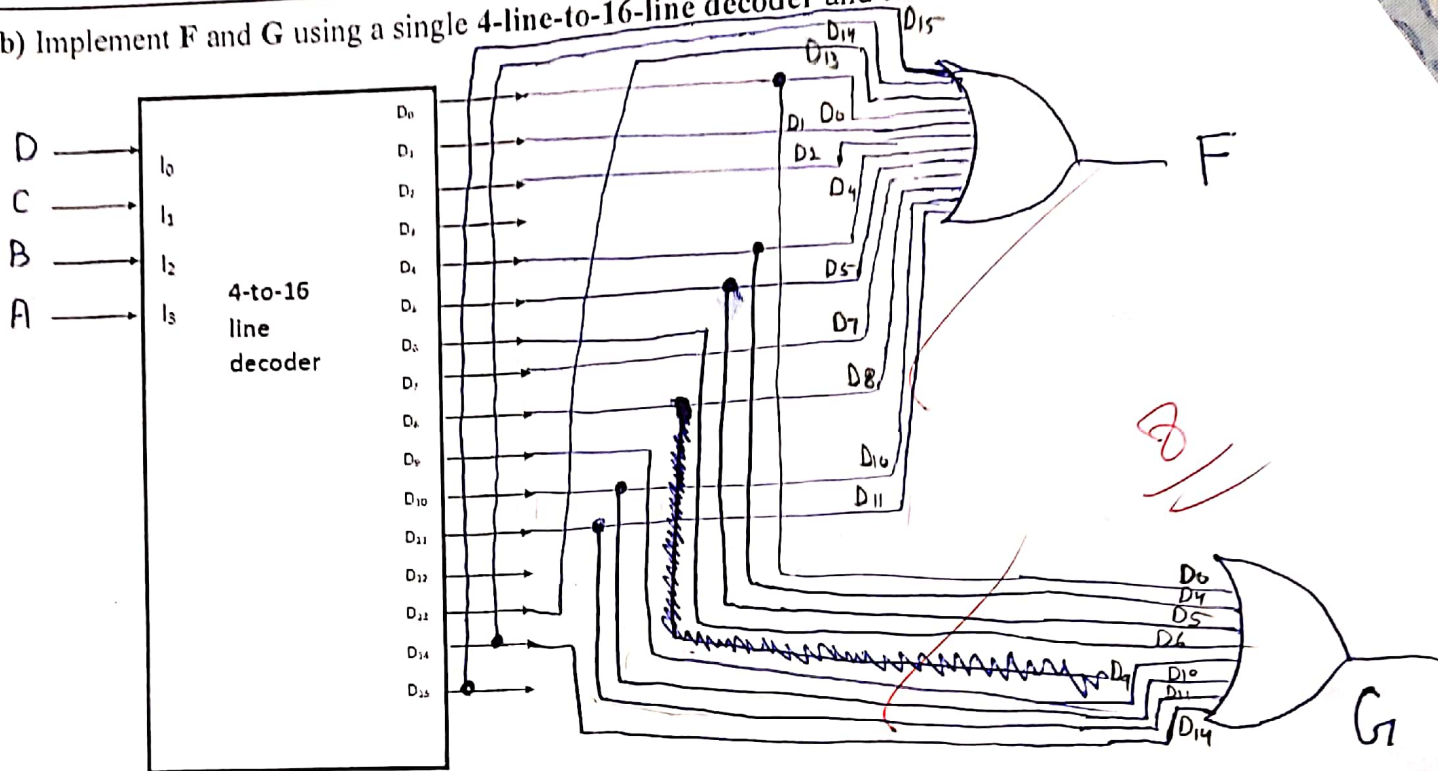(b) Implement F and G using a single 4-line-to-16-line decoder and two OR gates. [8]



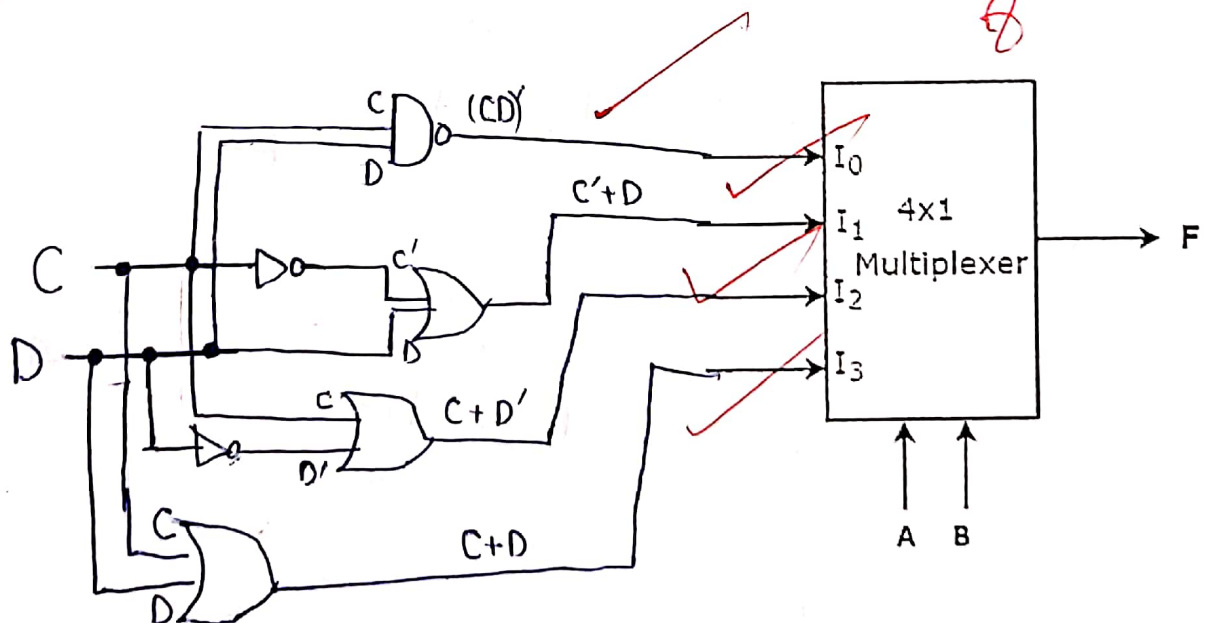(c) Implement the function F using 4 x 1 MUX and additional gates. [8]

[Note: you are not allowed to change the variables on the selection line]



# National University of Computer and Emerging Sciences, Lahore Campus



**Course:** Digital Logic Design  
**Program:** BS(Computer Science/ Data Science)  
**Duration:** 60 Minutes  
**Paper Date:** 24/03/2022  
**Section:** ALL  
**Exam:** Midterm-I

**Course Code:** EE1005  
**Semester:** Spring 2022  
**Total Marks:** 50  
**Weight:** 15%  
**Page(s):** 4  
**Roll No.:**

3/5  
-(2.5) = 34

**Section:**

- Instruction/Notes:**
- Attempt all the questions on this answer booklet.
  - Make sure to write down your roll # on EVERY sheet in the given space.
  - Use of calculator is not allowed.

**Question 1 [10 Marks]:** Determine the value of the radix  $r$  if  $(112)_r = (1012)_3$

$$\begin{aligned}
 (1 \times r^2) + (1 \times r^1) + (2 \times r^0) &= (1 \times 3^3) + (0 \times 3^2) + (1 \times 3^1) + (2 \times 3^0) \\
 r^2 + r + 2 &= 27 + 0 + 3 + 2 \\
 r^2 + r + 2 &= 32 \\
 r^2 + r + 2 - 32 &= 0 \\
 r^2 + r - 30 &= 0 \\
 r &= \frac{-1 \pm \sqrt{1^2 - 4(30)}}{2} \\
 r &= \frac{-1 \pm 11}{2} \\
 r &= \frac{11 - 1}{2} = 5
 \end{aligned}$$

10 ✓

**Question 2 [10 + 6 = 16 Marks]:** Design a combinational circuit with a 4-bit input. The 4-bit input represents the month number, 0001 for January, 0010 for February, 0011 for March and so on. The circuit has three outputs  $F_2, F_1, F_0$  as shown in Figure 1.

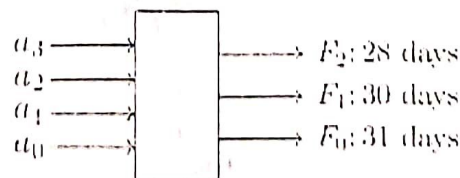


Figure 1: Number of days calculator.

25 + 5 + 2  
32



The output  $F_2$  is 1 if the input month has 28 days.

The output  $F_1$  is 1 if the input month has 30 days,

and output  $F_0$  is 1 if the input month has 31 days. Ignore the leap year.

For invalid inputs, it doesn't matter what's the output.

(a) Fill-in the entries for the outputs in the truth table shown below:

Inputs				Outputs		
$a_3$	$a_2$	$a_1$	$a_0$	$F_2$	$F_1$	$F_0$
0	0	0	0	X	X	X
Jan	0	0	1	0	0	1
Feb	0	1	0	0	1	0
March	0	1	1	0	0	1
April	0	1	0	1	0	0
M	0	1	1	0	0	1
J	0	1	1	0	0	1
J	0	1	1	0	0	1
A	1	0	0	0	0	1
S	1	0	1	1	0	0
O	1	0	1	0	0	1
N	1	0	1	1	0	0
Dec	1	1	0	0	0	1
13	1	1	0	X	X	X
14	1	1	1	X	X	X
15	1	1	1	X	X	X

7.5 + 2.5

J - 1  
F - 1  
M - 1  
A - 1  
M - 1  
J - 1  
J - 1  
A - 1  
S - 1  
O - 1  
N - 1

(b) Write the function  $F_2$  and  $F_0$  in Sum of Minterms form and  $F_1$  in Product of Maxterm form.

$$F_2(a_3, a_2, a_1, a_0) = \sum m(\underline{1, 3, 5, 7, 9, 11}, 4, 6, 9, 11) \quad \bar{A}\bar{D} + AD$$

$$F_1(a_3, a_2, a_1, a_0) = \prod M(\underline{1, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12}) \quad C + \bar{D} + \bar{B} + \bar{A}$$

$$F_0(a_3, a_2, a_1, a_0) = \sum m(\underline{4, 6, 9, 11}, 1, 3, 5, 7, 8, 10, 12) \quad \bar{A}D + A\bar{D}$$

$$\bar{C} + D + B + A$$

$$C + \bar{D} + \bar{B} + \bar{A}$$

School of Computer Science

CDBA

AB	CD	00	01	11	10
00	X	0	0	0	1
01	0	0	0	0	0
11	0	X	X	X	X
10	0	0	0	0	0

AB	CD	00	01	11	10
00	X	0	0	0	1
01	0	0	0	0	0
11	0	X	X	X	X
10	0	0	0	0	0

AB	CD	00	01	11	10
00	X	0	0	0	1
01	0	0	0	0	0
11	0	X	X	X	X
10	0	0	0	0	0



Question 3 [4 + 10 + 10 = 24 Marks]: A Boolean function is given as follows:

$$F(A, B, C, D) = AC' + B'D + A'CD + ABCD$$

a) Write down the function F in Sum of Minterms and Product of Maxterm form.

$$F(A, B, C, D) = \sum m(1, 3, 7, 9, 11, 12, 13, 15)$$

$$F(A, B, C, D) = \prod M(0, 2, 4, 5, 6, 10, 14)$$

b) Minimize the function F in Sum of Products form using K-maps shown below:

AB \ CD	00	10	11	01
00	0	1	1	0
10	0	0	1	0
11	1	1	1	0
01	1	1	1	0

$$F(A, B, C, D) = \underline{B\bar{D} + BC + \bar{A}C + \bar{B}CD}$$

$$\begin{aligned} & (AC') + B'D + A'CD + ABCD \\ & A'CD(B+B') + \overset{1111}{2^3 2^2 2^1 2^0} \\ & A'CDB + A'B'CD + 15 \end{aligned}$$

$$\begin{aligned} & 0111 \quad A'B\bar{C}D \\ & 0111 \quad \boxed{m_7} \\ & 0011 \quad \boxed{m_3} \quad \boxed{m_{15}} \end{aligned}$$

$$AC'(B+B')(D+D')$$

$$(AC'B + AB'C')(D+D')$$

$$AB\bar{C}D + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D}$$

c) Minimize the function F in Product of Sums form using K-maps shown below:

AB \ CD	00	10	11	01
00	0	1	1	0
10	0	0	1	0
11	1	1	1	0
01	1	1	1	0

$$\begin{aligned} & 1101 \quad 1100 \quad 1001 \\ & \boxed{m_3} \quad \boxed{m_2} \quad \boxed{m_8} \quad \boxed{m_9} \end{aligned}$$

$$B'D(A+A')(C+C')$$

$$F(A, B, C, D) = \underline{(C + \bar{D})(B + C)(\bar{A} + B + D)}$$




Course: Digital Logic Design  
 Program: BS (Computer Science)  
 Duration: 10 Minutes  
 Paper Date: 13-03-2022  
 Section: N  
 Exam: Quiz 2

Course Code: EE1005  
 Semester: Spring 2022  
 Total Marks: 10  
 Weight: 1  
 Page(s): 1  
 Reg. No.

9.5

Instruction/Notes: Plagiarism will be dealt seriously causing an F in course

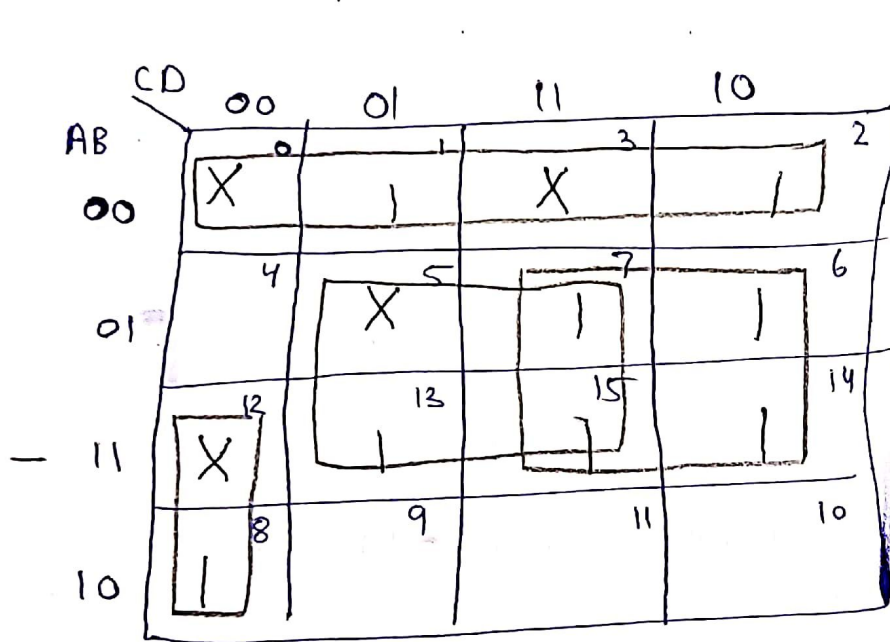Q1. Minimise the following function in SOP minimal form using K-Maps:  
 $F(A, B, C, D) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)$



$$\begin{array}{cccc} 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ \hline & A & \bar{C} & D \end{array}$$

$$AB + \bar{A}D + \bar{A}C + \bar{C}D$$

$$\begin{array}{cccc} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & 0 \\ \hline & \bar{A} & \bar{B} & \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 0 & 1 \\ 0 & 1 & 1 & 1 \\ 1 & 1 & 0 & 1 \\ 1 & 1 & 1 & 1 \\ \hline & B & D & \end{array}$$

$$\begin{array}{cccc} 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 \\ 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 0 \\ \hline & B & C & \end{array}$$

$$\begin{array}{cccc} 1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ \hline & A & \bar{C} & \bar{D} \end{array}$$

9.5

$$\bar{A}\bar{B} + BD + BC + A\bar{C}\bar{D}$$



Course: Digital Logic Design  
 Program: BS (Computer Science)  
 Duration: 10 Minutes  
 Paper Date: 07-03-2022  
 Section: N  
 Exam: Quiz 1

Course Code: EE1005  
 Semester: Spring 2022  
 Total Marks: 10  
 Weight: 1  
 Page(s): 1  
 Reg. No.:

Instruction/Notes: Plagiarism will be dealt seriously causing an F in course

Solve  $(72)_8 \times (12)_8 = (1104)_8$

$$\begin{array}{r} 72 \\ 12 \\ \hline 1164 \\ 72 \times \\ \hline 1104 \end{array}$$

$$\begin{array}{r} 8 \overline{) 14} \\ 8 \overline{) 1} - 6 \uparrow \\ 0 \quad 1 \end{array}$$

$$\begin{array}{r} 8 \overline{) 8} \\ 8 \overline{) 1} - 0 \\ 0 \quad - 1 \end{array}$$

$$\begin{array}{r} 8 \overline{) 9} \\ 8 \overline{) 1} - 1 \\ 0 \quad 1 \end{array}$$

Solve  $(27)_8 + (8)_{10} = (1F)_{16}$

$$\begin{aligned} (27)_8 &= (2 \times 8^1) + (7 \times 8^0) \\ &= (23)_{10} \end{aligned}$$

$$(2 \times 8^1) + (7 \times 8^0) = 16 + 56 = 72$$

$$(72)_{10} + (8)_{10} = (80)_{10} \quad (23)_{10} + (8)_{10} = (31)_{10}$$

$$\begin{array}{r} 16 \overline{) 576} \\ 16 \overline{) 32} - 0 \uparrow \\ 16 \overline{) 2} - 4 \\ 0 \quad - 2 \end{array}$$

$$\begin{array}{r} 16 \overline{) 80} \\ 16 \overline{) 5} - 0 \uparrow \\ 0 \quad - 5 \end{array}$$

$$\begin{array}{r} 16 \overline{) 31} \\ 16 \overline{) 1} - F \\ 0 \quad - 1 \end{array}$$

$$(240)$$

A  
B  
C  
D  
E  
F

$$\begin{array}{r} 16 \\ 16 \\ \hline 23 \\ 8 \end{array}$$